
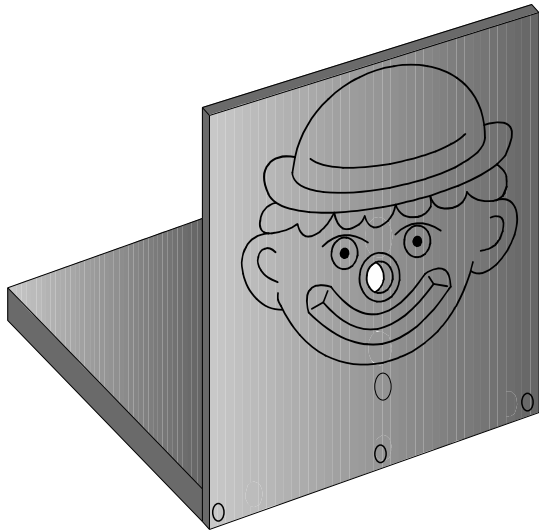


# CIRCUIT CLOWNS

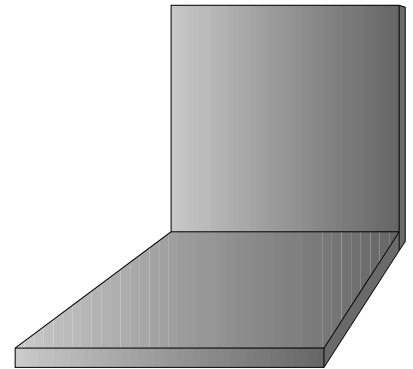1. Using correx and wood build a simple structure to support your clown template.
2. Stick the clowns face to the board.



3. Pierce a hole through the board to show the position of the nose bulb and bow tie.

4. Build a circuit as in the diagram below. Try to make a switch with drawing pins and paper clips.

